
SONET Bidirectional Line-Switched Ring Equipment Generic Criteria

Contents

1. Introduction.....	1-1
1.1 Update History	1-2
1.2 Scope.....	1-4
1.3 Criteria.....	1-5
1.4 Requirement Labeling Conventions.....	1-5
1.4.1 Numbering of Requirement and Related Objects	1-5
1.4.2 Requirement, Conditional Requirement, and Objective Object Identification	1-6
1.5 Organization.....	1-6
1.6 Source Documents	1-7
1.7 Assumptions.....	1-7
2. Definitions, Terminology, and Common Phrases.....	2-1
3. Overview of the BLSR Architecture.....	3-1
3.1 Two-Fiber BLSR Overview	3-2
3.2 Four-Fiber BLSR Overview.....	3-16
3.3 VT-Access Overview	3-23
3.4 Extra Traffic Overview	3-30
3.4.1 Squelching to Avoid Misconnected Traffic.....	3-30
3.5 Enhanced Non-preemptible Unprotected Traffic (E-NUT) Overview	3-36
3.6 STS Squelching Logic Overview.....	3-38
3.6.1 Squelching for Unidirectional (and Bidirectional) Circuits.....	3-38
3.6.2 Squelching for Multiply Sourced/Dropped Unidirectional Circuits.....	3-40
3.7 Ring Interworking Overview	3-44
3.7.1 Drop-and-Continue Method.....	3-44
3.7.2 Protection Switching Mechanisms for Inter-ring Traffic.....	3-47
3.7.2.1 Interconnection Survivability with Drop and Continue on Working Bandwidth Channels.....	3-48
3.7.2.2 Interconnection Survivability with Drop and Continue on Protection Bandwidth (Ring Interworking on Protection)	3-49
3.7.2.3 Cable Cut in Ring #1 and Ring #2.....	3-54
3.7.2.4 Primary Node Failure in Ring #1 and Cable Cut in Ring #2	3-55
3.7.3 Dual Transmit Method.....	3-57
3.7.3.1 Dual Transmit On Working Channels	3-57
3.7.3.2 Dual Transmit On Protection Channels.....	3-58

4. Network Applications	4-1
5. Functions Needed for NE Deployment in a BLSR	5-1
6. Equipment Criteria and K1/K2 Byte Protocol	6-1
6.1 Equipment Criteria	6-1
6.1.1 Equipment Criteria for 2- and 4-Fiber Ring.....	6-1
6.1.2 Equipment Criteria for 4-Fiber BLSRs Only	6-7
6.1.3 Equipment Criteria for 2-Fiber BLSRs Only	6-7
6.2 Switch Initiation and K1 and K2 Protocol	6-8
6.2.1 Switch Initiation Criteria.....	6-8
6.2.1.1 Externally Initiated Protection Switching Commands (OS or WS).....	6-9
6.2.1.2 Automatically Initiated Protection Switch Requests	6-12
6.2.1.3 Functional Requirements	6-14
6.2.2 Bit-Oriented Protocol for K1/K2 Bytes	6-15
6.2.2.1 Steady State Behavior.....	6-19
6.2.2.2 State Transition Rules.....	6-27
6.2.2.3 Examples of Protection Switching in a BLSR.....	6-42
7. Requirements for Ring Interconnection	7-1
7.1 Ring Interconnection Using Protection Capacity.....	7-9
7.2 Dual Transmit Method	7-11
8. Operations, Administration, Maintenance, and Provisioning (OAM&P) Criteria ...	8-1
8.1 Operations Data Networking.....	8-1
8.2 Alarm Surveillance Requirements	8-2
8.2.1 Troubles in the APS Channel.....	8-3
8.2.2 Additional Information Needed in BLSR	8-5
8.2.3 BLSRs and Routine Operations	8-6
8.3 Performance Monitoring (PM).....	8-7
8.4 Testing and Control Functions	8-9
8.5 Memory Administration.....	8-12
9. System Availability Criteria.....	9-1
10. Synchronization Criteria	10-1
Requirement-Object List	ROL-1
Requirement-Object Index	ROI-1
References	References-1
Acronyms.....	Acronyms-1

List of Figures

Figure 2-1.	Isolated Node	2-11
Figure 2-2.	Short and Long Paths	2-11
Figure 2-3.	Ring Segmentation	2-12
Figure 2-4.	Service Selector (Interconnection Between Two BLSRs)	2-13
Figure 3-1.	Traffic Flow Support on a BLSR Ring	3-1
Figure 3-2.	Simplified Node in a 2-Fiber BLSR	3-3
Figure 3-3.	4-Node, 2-Fiber BLSR	3-4
Figure 3-4.	Traffic Assignment Illustration for a 2-Fiber BLSR	3-5
Figure 3-5.	Dropped and Continued Paths	3-7
Figure 3-6.	Ring Switching for a Unidirectional Degradation on a 2-Fiber BLSR	3-8
Figure 3-7.	Node Failure on a 2-Fiber BLSR.....	3-10
Figure 3-8.	Misconnection for STS-1 #1 for Traffic from Node 4 to Node 1.....	3-11
Figure 3-9.	Misconnection for STS-1 #1 for Traffic from Node 2 to Node 1.....	3-12
Figure 3-10.	Misconnection for STS-1 #2 for Traffic from Node 3 to Node 1.....	3-13
Figure 3-11.	Misconnection for STS-1 #3 for Traffic from Node 4 to Node 1.....	3-14
Figure 3-12.	Isolation of Two Nodes by a Cable Cut	3-15
Figure 3-13.	Simplified Node in a 4-Fiber BLSR	3-17
Figure 3-14.	4-Node, 4-Fiber BLSR	3-18
Figure 3-15.	Unidirectional Span Failure on a 4-Fiber BLSR	3-19
Figure 3-16.	Cable Cut on a 4-Fiber BLSR.....	3-20
Figure 3-17.	Restoration for a Cable Cut on a 4-Fiber BLSR.....	3-21
Figure 3-18.	Cable Cut and a Span Switch on a 4-Fiber BLSR (Before a Ring Switch)	3-22
Figure 3-19.	Misconnection of Traffic Related to Existing Switches.....	3-23
Figure 3-20.	VT Squelch Table Example (Bidirectional Traffic) — All Nodes VT- access	3-26
Figure 3-21.	VT Squelch Table Example (Unidirectional Traffic) — Not All Nodes VT- access	3-27
Figure 3-22.	VT Squelch Table Example (Inter-Ring Capability) — All Nodes VT- access	3-29
Figure 3-23.	Example of Potential for Misconnection	3-31
Figure 3-24.	Signalling during SF-R with Extra Traffic	3-33
Figure 3-25.	Signalling during SF-S with Extra Traffic	3-35
Figure 3-26.	Conceptual Representation of a E-NUT Table	3-37
Figure 3-27.	Unidirectional Circuit Squelching Example Where the Failure is in the Opposite Direction from the Unidirectional Circuit.....	3-38
Figure 3-28.	Unidirectional Circuit Squelching Example Where the Failure is in the Direction of the Unidirectional Circuit.....	3-39
Figure 3-29.	Bidirectional Circuit Squelching Example	3-40
Figure 3-30.	Multiply Sourced Unidirectional Circuit Squelching Example where the Failure is in the Opposite Direction from the Unidirectional Circuit.....	3-41

Figure 3-31.	Multiply Dropped Unidirectional Circuit Squelching Example where the Failure is in the Opposite Direction from the Unidirectional Circuit.....	3-41
Figure 3-32.	Multiply Sourced Unidirectional Circuit Squelching Example where the Failure is in the Direction of the Unidirectional Circuit.....	3-42
Figure 3-33.	Multiply Dropped Unidirectional Circuit Squelching Example where the Failure is in the Direction of the Unidirectional Circuit.....	3-42
Figure 3-34.	Bidirectional Circuit Squelching Example with Multiply Sourced and Multiply Dropped Traffic	3-43
Figure 3-35.	Baseline Ring Interconnection.....	3-45
Figure 3-36.	Interconnection of BLSR and Mesh Network	3-46
Figure 3-37.	Correlation Between Inter-ring Circuit and Multiply Sourced and Multiply Dropped Circuits.....	3-48
Figure 3-38.	Squelch Table Example for Inter-ring Traffic with Secondary Circuit on Working Bandwidth	3-49
Figure 3-39.	Ring Interworking on Protection	3-50
Figure 3-40.	Opposite-Side Routing with (1) Service Circuit on Protection and (2) Service Circuit on Working: Double Link Failures.....	3-51
Figure 3-41.	Squelch Table Example for Inter-ring Traffic with Secondary Circuit on Protection Bandwidth	3-52
Figure 3-42.	RIP Table Example for Inter-ring Traffic with Secondary Circuit on Protection Bandwidth	3-52
Figure 3-43.	Primary Node Failure Restoral in a BLSR with Secondary Circuit on Protection: Basic Operation.....	3-53
Figure 3-44.	Link Failure Restoral in a BLSR with Secondary Circuit on Protection: Optional Enhanced Operation	3-53
Figure 3-45.	Cable Cut in Ring #1 and Ring #2.....	3-54
Figure 3-46.	Primary Node Failure in Ring #1 and Cable Cut in Ring #2 with Optional Enhanced Operation	3-55
Figure 3-47.	Primary Node Failure in Ring #1 and Cable Cut in Ring #2 with Basic Secondary Node Operation.....	3-56
Figure 3-48.	Dual transmit Ring Interworking - Relieved Congestion P-S	3-58
Figure 3-49.	Dual Transmit Ring Interworking - Improved Bandwidth Efficiency ...	3-59
Figure 3-50.	BLSR Interconnection with Dual Transmit and Same Side Routing	3-60
Figure 3-51.	BLSR Interconnection with Dual Transmit and Opposite Side Routing	3-61
Figure 6-1.	Isolated Node Signaling (Signaling States Before B and D Establish a Ring Bridge and Switch)	6-24
Figure 6-2.	Four-Fiber BLSR - Unidirectional Failure (Span) on Working From E to F. 6-52	
Figure 6-3.	Four-Fiber BLSR - Unidirectional Failure (Span) on Working From E to F (Concluded)	6-54
Figure 6-4.	Two- or Four-Fiber BLSR - Unidirectional SF (Ring).....	6-55
Figure 6-5.	Two- or Four-Fiber BLSR - Unidirectional SF (Ring) (Concluded).....	6-57
Figure 6-6.	Two- or Four-Fiber BLSR - Bidirectional SF (Ring).....	6-58
Figure 6-7.	Two- or Four-Fiber BLSR - Bidirectional SF (Ring) (Concluded).....	6-60

Figure 6-8.	Two- or Four-Fiber BLSR - Unidirectional SD (Ring).....	6-61
Figure 6-9.	Two- or Four-Fiber BLSR - Node Failure.....	6-63
Figure 6-10.	Two- or Four-Fiber BLSR - Node Failure (Concluded).....	6-65
Figure 6-11.	Four-Fiber BLSR - Unidirectional Signal Fail (Ring) Pre-empting a Unidirectional Signal Degrade (Span) on Non-Adjacent Spans	6-66
Figure 6-12.	Four-Fiber BLSR - Unidirectional Signal Fail (Ring) Pre-empting a Unidirectional Signal Degrade (Span) on Non-Adjacent Spans (Concluded) 6-68	6-68
Figure 6-13.	Four-Fiber BLSR - Unidirectional Signal Fail (Ring) Pre-empting a Unidirectional Signal Degrade (Span) on Adjacent Spans.....	6-69
Figure 6-14.	Four-Fiber BLSR - Unidirectional Signal Fail (Ring) Pre-empting a Unidirectional Signal Degrade (Span) on Adjacent Spans (Concluded).....	6-71
Figure 6-15.	Four-Fiber BLSR - Unidirectional Signal Fail (Span) Pre-empting a Unidirectional Signal Fail (Ring) on Adjacent Spans	6-72
Figure 6-16.	Two- or Four-Fiber BLSR - Unidirectional Signal Fail (Ring) Plus Unidirectional Signal Fail (Ring) on Non-Adjacent Spans	6-74
Figure 6-17.	Two- or Four-Fiber BLSR - Node Failure on a Ring with VT access ...	6-76
Figure 6-18.	Two- or Four-Fiber BLSR - Node Failure on a Ring with VT access (Concluded)	6-77
Figure 6-19.	Two- or Four-Fiber BLSR - Node Failure on a Ring with VT access and Extra Traffic	6-78
Figure 6-20.	Two- or Four-Fiber BLSR - Node Failure on a Ring with VT access and Extra Traffic (Concluded)	6-79
Figure 7-1.	Interconnection between Two BLSRs (Same-side Routing).....	7-2
Figure 7-2.	Interconnection between Two BLSRs (Opposite-side Routing)	7-3
Figure 7-3.	Primary Node Failure on a BLSR.....	7-4
Figure 7-4.	Interconnection of a BLSR with a UPSR	7-5
Figure 7-5.	Service Selection in the Presence of STS PDI-P and STS-SD.....	7-8
Figure 8-1.	Protection Switch Counts: 2-Fiber BLSR	8-8
Figure 8-2.	Protection Switch Counts: 4-Fiber BLSR	8-8
Figure 8-3.	Squelch Table Example (Based on Table 3-1)	8-13

List of Tables

Table 3-1.	Traffic Assignments on a 2-Fiber BLSR.....	3-6
Table 3-2.	Interconnection Options Between Two BLSRs.....	3-47
Table 6-1.	K1 Bit Assignments.....	6-17
Table 6-2.	K2 Bit Assignments.....	6-18
Table 6-3.	Relationships Between K2 Bit 5 and K1 Bits 1-4	6-19
Table 6-4.	Byte K1 and K2 Values Sourced in the Idle State.....	6-20
Table 6-5.	Default APS Codes	6-20
Table 6-6.	Byte K1 and K2 Values Sourced in the Switching State.....	6-21
Table 6-7.	SD-P and SF-P (LP-S) Coexisting with Ring Switches on the Same Span ... 6-22	
Table 7-1.	Hierarchy of Conditions for Service Selection.....	7-7